

NJU6676

Application Note

New Japan Radio Co., Ltd.

Frame Frequency

-Using the Built-in Oscillator(CLS="H")

$$f_{FR} \text{ (Frame Frequency)} = f_{OSC}/(4 \times 65)$$

$$f_{CL} \text{ (display clock)} = f_{OSC}/4$$

Ex. $f_{OSC} = 22\text{KHz}$

$$f_{FR} = 84.6 \text{ Hz}$$

$$f_{CL} \text{ (output)} = 5.5\text{KHz}$$

-Using a External Oscillator and the Built-in Voltage Booster (CLS="H", external clock signal inputted into OSC1 pin)

$$f_{FR} = OSC1/(4 \times 65)$$

$$f_{CL} \text{ (output)} = f_{OSC}/4$$


-Using External Oscillator and Power Supply (CLS="L", external clock signal inputted into CL pin)

$$f_{FR} = f_{CL}/65$$

$$f_{CL} \text{ (input)} = CL$$

LCD Bias Voltage Generator

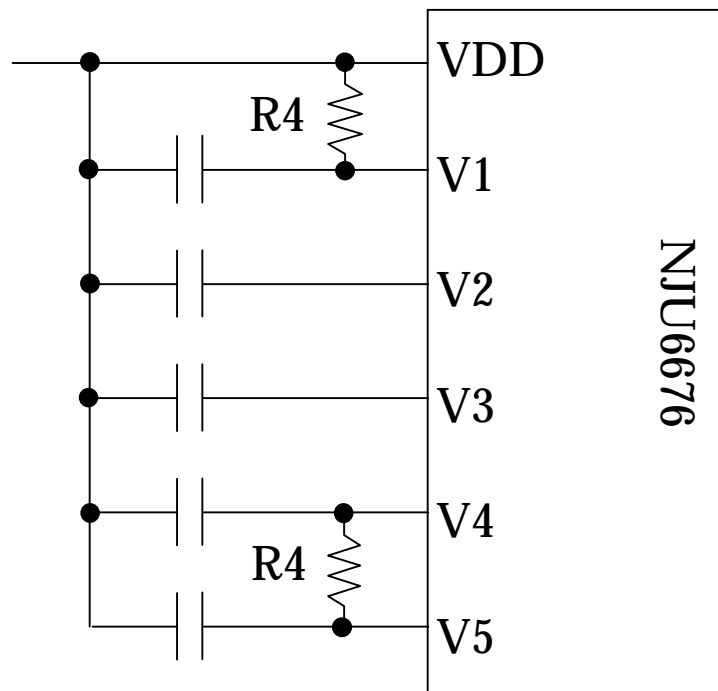When the built-in power supply circuit is used, for big panel, because the alternating and direct current consumption is bigger than the small one's, the bias voltage V1 and V4 is susceptible to change. To stabilize V1 and V4, the external resistors connecting like below is recommended. About resistor's value , please confirm with your practical application.




For reference: $R4 = 68K\Omega \sim$
(by our testing $R4$ is from $68K\Omega$ to $150K\Omega$)

New Japan Radio Co., Ltd.

Refresh Display

To stabilize the display, please refresh the instruction and display data at a constant frequency.

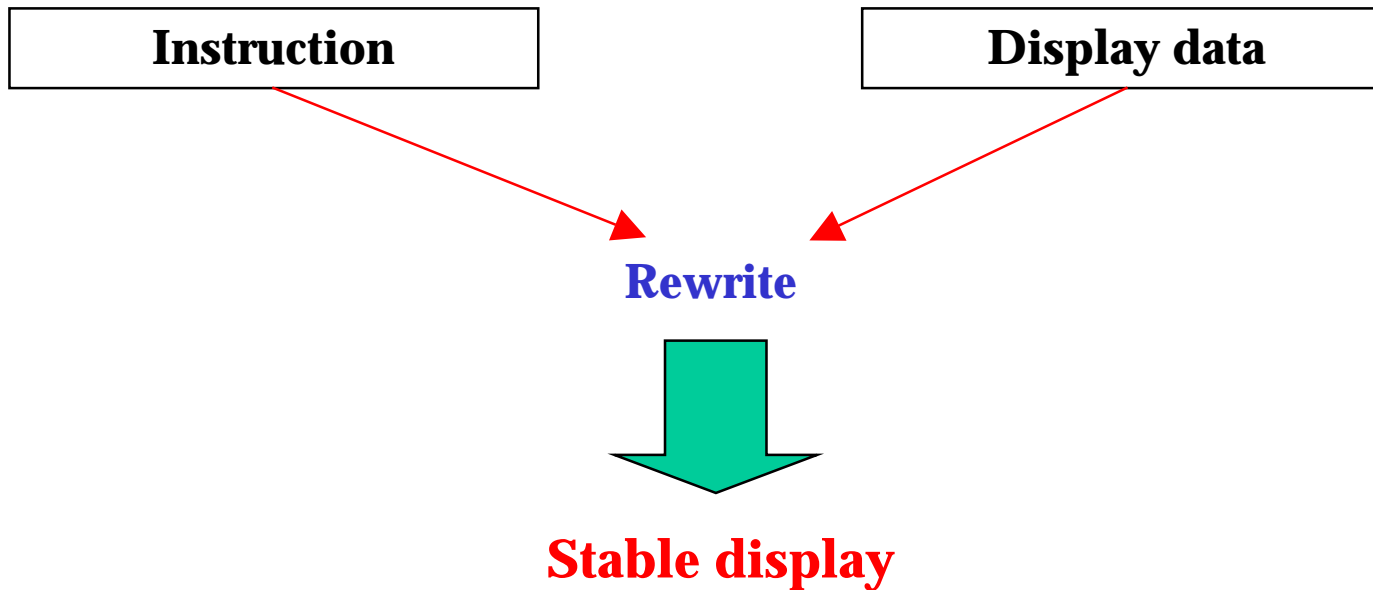
Further more, if the reset instruction data is the same as before, there is no effect on display.



Voltage Regulator

The built-in Voltage Booster generates V_{out} , then V_{out} is regulated by the Voltage Regulator and outputted as V_5 .

 The LCD driving voltage $VLCD (= VDD - V_5)$ can be adjusted by external R_a and R_b . No matter how the built-in voltage booster is set, it is impossible to obtain $VLCD$ higher than V_{out} .




For R_a and R_b , because they are directly connected to $VDD - V_5$, if the resistance is not big enough, the current consumption will increase. Reference value: $R_a + R_b = 1M\Omega \sim 5M\Omega$.


New Japan Radio Co., Ltd.

Sequence of Power ON/OFF(1)

- Power ON

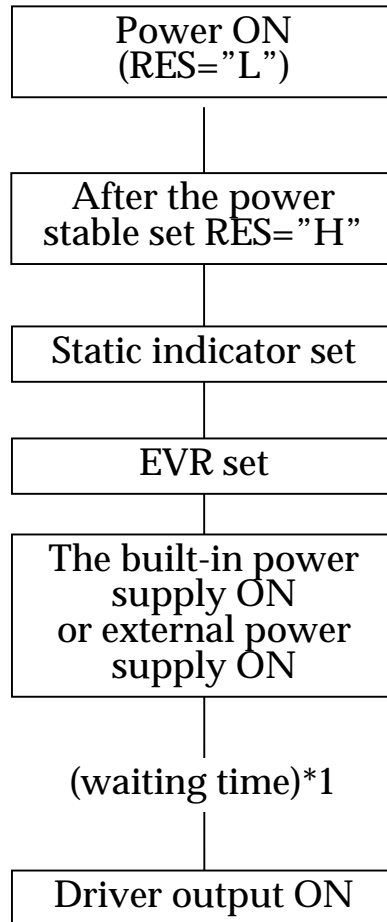

- Power OFF

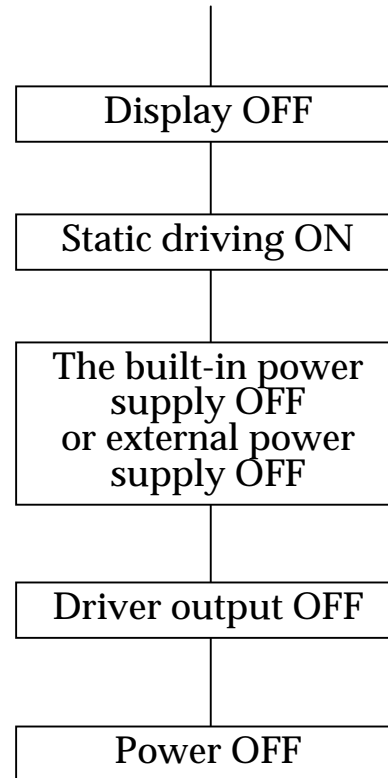

*1: The waiting time for the built-in power supply stabilizing will vary with the C_{OUT} , $C_1 \sim C_8$, V_{DD} , and V_{LCD} . Please confirm with practical application.

Sequence of Power ON/OFF(2)


If electrons are left in the stabilizing capacitor, which are connected to V1~V5 pins, when the power ON/OFF, unexpected pixels maybe turned on for a time. This is because the discharge speed of the capacitors is different, result in the order change of the bias voltage V1~V5.

There for, if there is unexpected lighting pixels during power ON, set a waiting time before the driver outputting signal.

If there is unexpected lighting pixels during power OFF, insert a resistor between VDD and slowly discharging pin.

The resistance and waiting time will change a lot with different LCM, please confirm with practical application.

 The figure shows that if V3 discharging speed is slow during power OFF, connect VDD and V3 with a 500K Ω ~ 5M Ω .



Specification of Oscillation Frequency


-Oscillation Frequency

	Min.	Typ.	Max.	
fOSC	18	22	26	[kHz]

-Frame Frequency = $f_{OSC}/(4 \times 65)$

	Min.	Typ.	Max.	
Frame Frequency	69.2	84.6	100	[Hz]

|----- -18% -----|----- 18% -----|

 

To avoid flicker phenomena, let frame frequency away from 50Hz~60Hz.

New Japan Radio Co., Ltd.